

DC Electrical Circuits

Chapter 28


Electromotive Force

Potential Differences

Resistors in Parallel and Series

Circuits with Capacitors


Resistors in Series

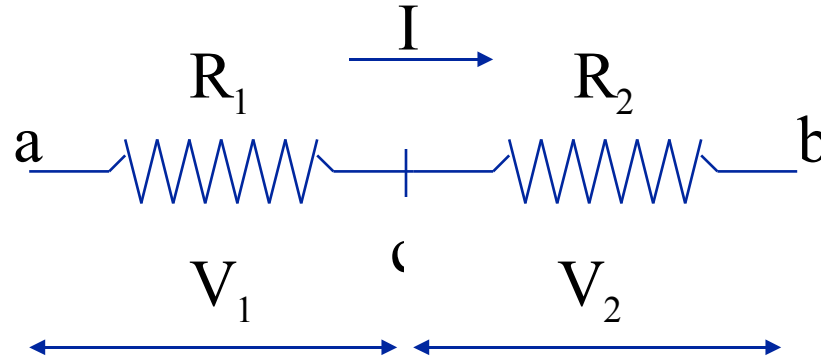

The pair of resistors, R_1 and R_2 , can be replaced by a single equivalent resistor R ; one which, given I , has the same total voltage drop as the original pair.

Note: the current I is the same, anywhere between a and b , but there is a voltage drop V_1 across R_1 , and a voltage drop V_2 across R_2 .


Resistors in Series

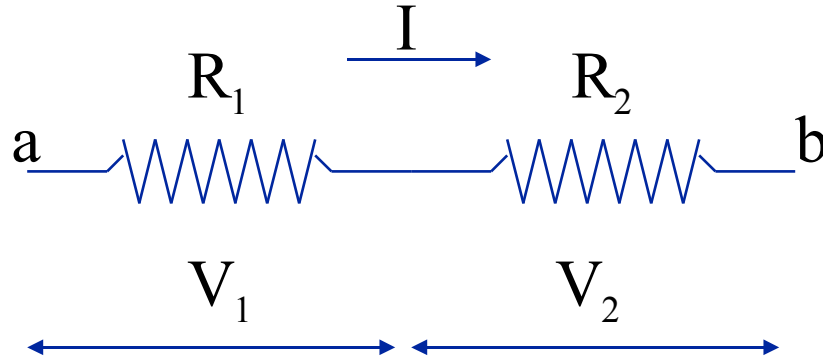

The pair of resistors can be replaced by a single equivalent resistor R_{eq} ; one which, given I , has the same total voltage drop as the original pair.

$$V = V_1 + V_2 = I R_1 + I R_2$$

Resistors in Series

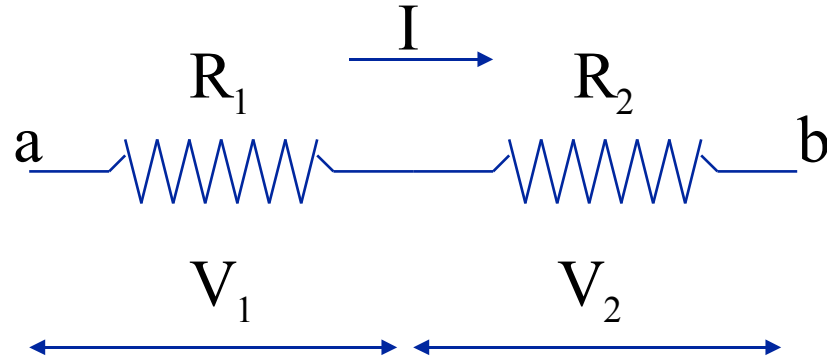


The pair of resistors can be replaced by a single equivalent resistor R_{eq} ; one which, given I , has the same total voltage drop as the original pair.

$$V = V_1 + V_2 = I R_1 + I R_2$$

We want to write this as $V = I R_{eq}$

Resistors in Series

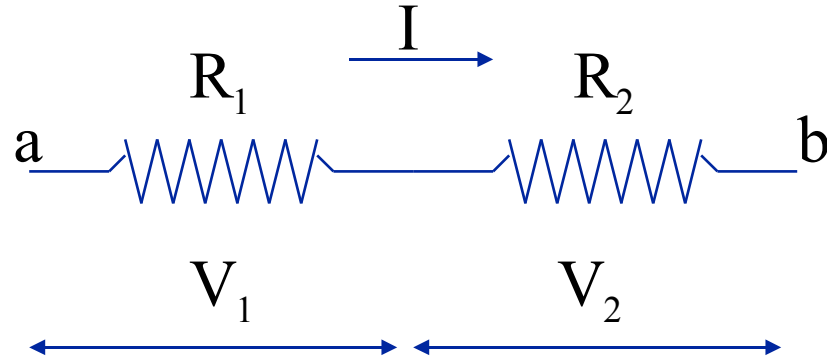


The pair of resistors can be replaced by a single equivalent resistor R_{eq} ; one which, given I , has the same total voltage drop as the original pair.

$$V = V_1 + V_2 = I R_1 + I R_2$$

We want to write this as $V = I R_{eq}$

hence $R_{eq} = R_1 + R_2$

Resistors in Series

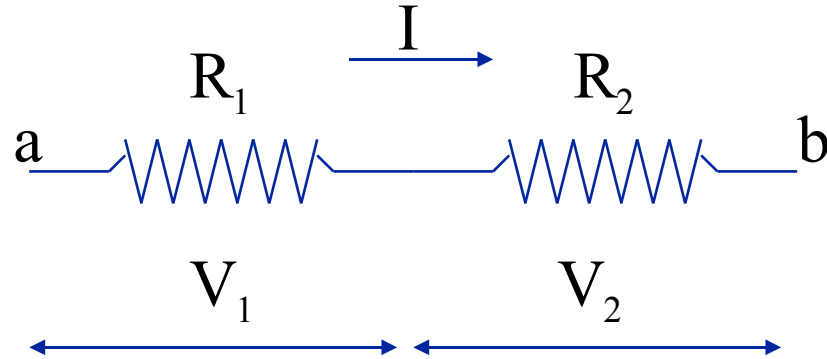


What is the voltage drop across each resistor ?

$$V_1 = I R_1 \text{ but } I = V / (R_1 + R_2) \Rightarrow V_1 = V R_1 / (R_1 + R_2)$$


$$V_2 = I R_2 \text{ but } I = V / (R_1 + R_2) \Rightarrow V_2 = V R_2 / (R_1 + R_2)$$

Resistors in Parallel

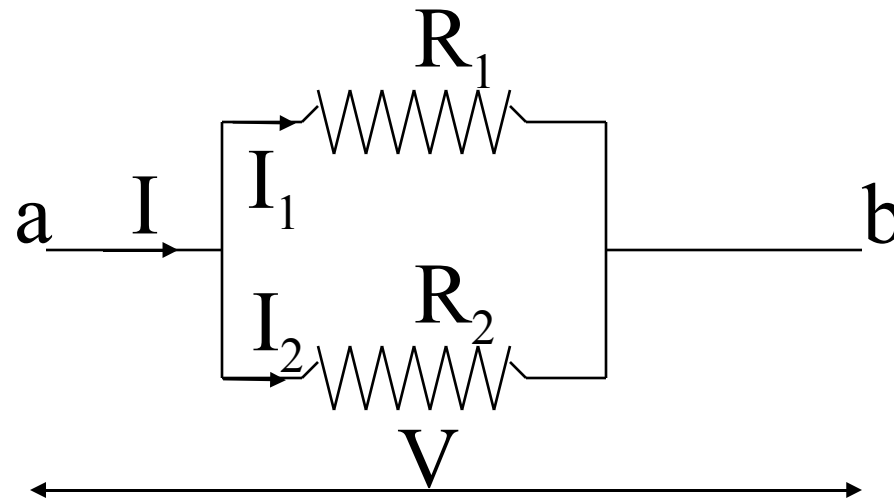

Again find the equivalent single resistor which has the same V if I is given.


Resistors in Parallel

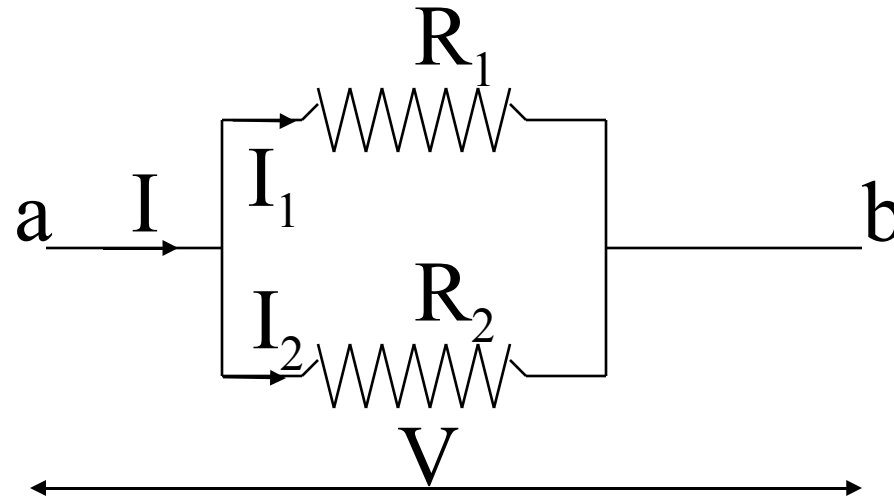

Again find the equivalent single resistor which has the same V if I is given. Here the total I splits:

$$I = I_1 + I_2 = V / R_1 + V / R_2 = V(1 / R_1 + 1 / R_2)$$

Resistors in Parallel

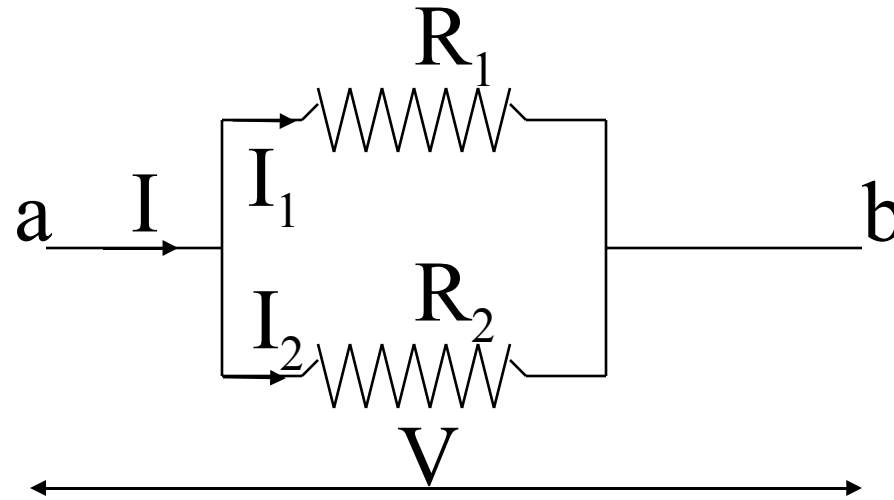


Again find the equivalent single resistor which has the same V if I is given. Here the total I splits:

$$I = I_1 + I_2 = V / R_1 + V / R_2 = V(1 / R_1 + 1 / R_2)$$

We want to write this as: $I = V / R_{eq}$

Resistors in Parallel

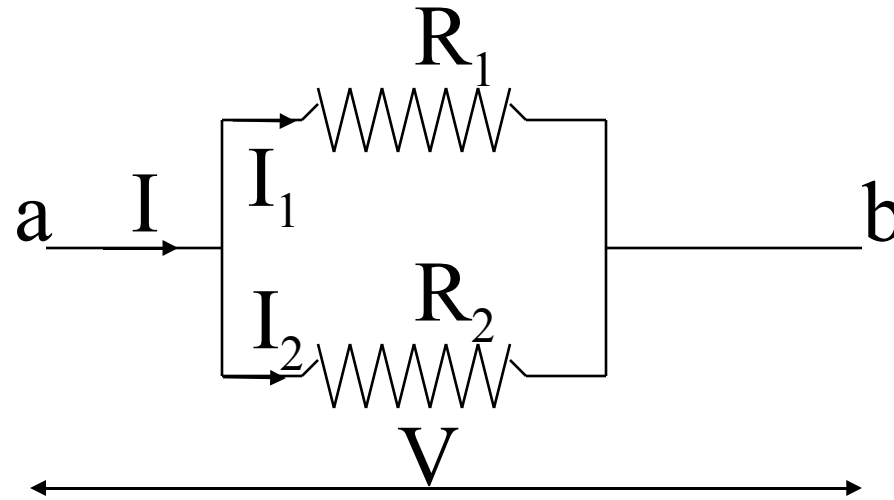



Again find the equivalent single resistor which has the same V if I is given. Here the total I splits:

$$I = I_1 + I_2 = V / R_1 + V / R_2 = V(1 / R_1 + 1 / R_2)$$

We want to write this as: $I = V / R_{eq}$

Hence $1 / R_{eq} = 1 / R_1 + 1 / R_2$

Parallel and Series

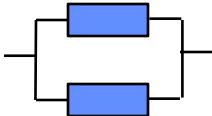
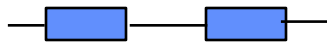
	Resistors	Capacitors
Parallel 	$1/R = 1/R_1 + 1/R_2$	$C = C_1 + C_2$
Series 	$R = R_1 + R_2$	$1/C = 1/C_1 + 1/C_2$

Batteries and Generators

- Current is produced by applying a potential difference across a conductor ($I=V/R$) [This is not equilibrium so there is an electric field inside the conductor].
- This potential difference is set up by some source, such as a battery or generator [that generates charges, from some other type of energy, *i.e.* chemical, solar, mechanical].
- Conventionally an “applied voltage” is given the symbol E (units: volts).
- For historical reasons, this applied voltage is often called the “electromotive force” (**emf**) [even though it’s not a force].

The Voltaic Pile


Volta's original battery

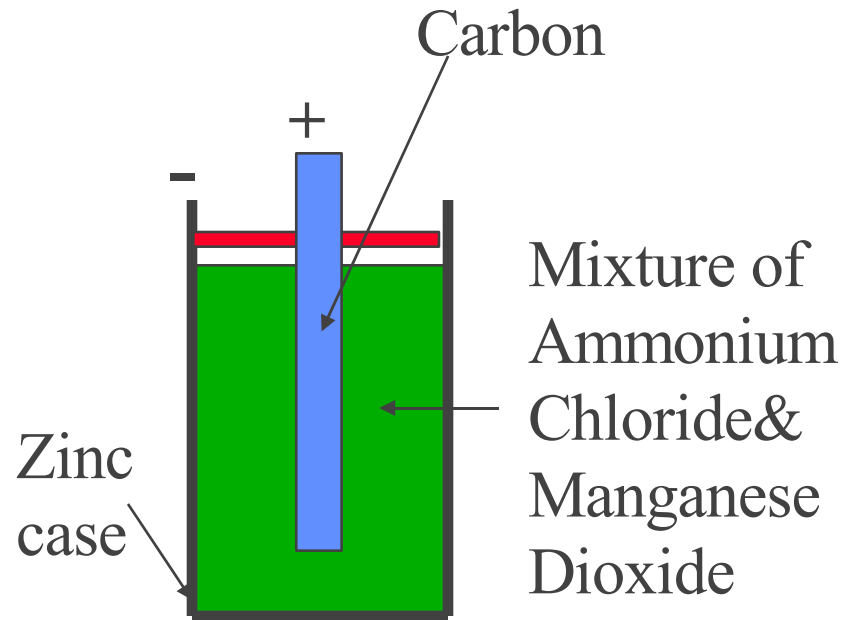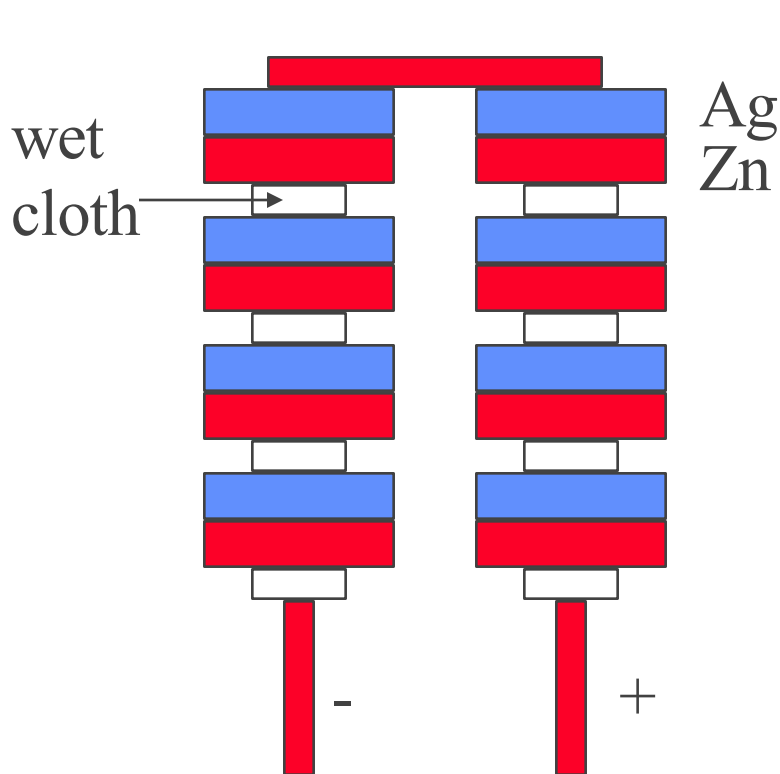

electrical converter...


.....converts chemical energy to electrical energy

Electrical Description of a Battery

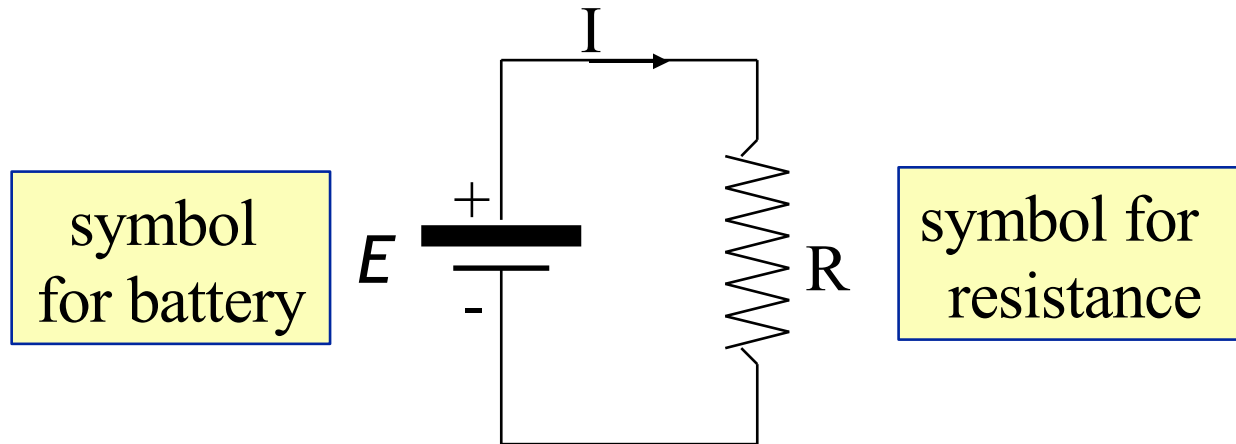

- **A battery does work on positive charges in moving them to higher potential (inside the battery).**
- **The EMF E , most precisely, is the work per unit charge exerted to move the charges “uphill” (to the + terminal, inside)**
- **... but you can just think of it as an “applied voltage.”**
- **Current will flow, in the external circuit, from the + terminal, to the – terminal, of the battery.**


Resistors in Series

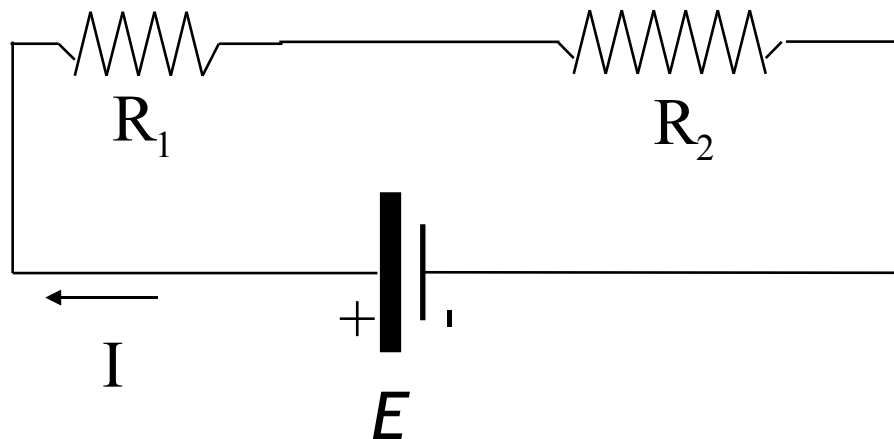

Given $R_{\text{eq}} = R_1 + R_2$, the current is $I = E / (R_1 + R_2)$

One can then work backwards to get the voltage across each resistor:

Resistors in Series

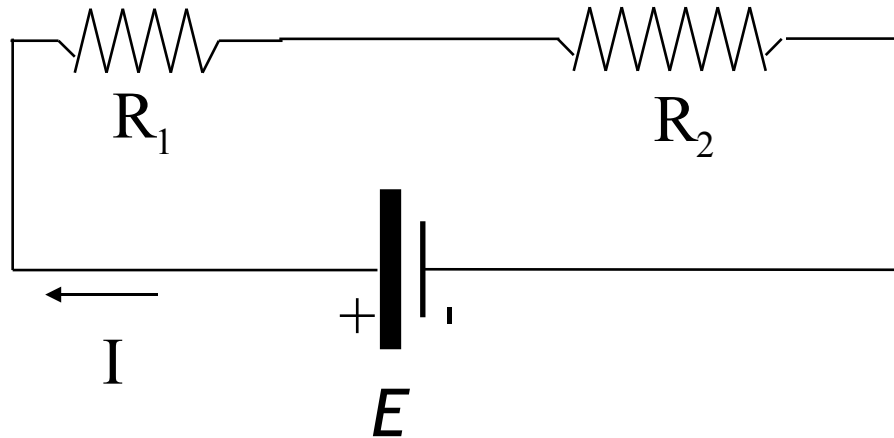


Given $R_{\text{eq}} = R_1 + R_2$, the current is $I = E / (R_1 + R_2)$

One can then work backwards to get the voltage across each resistor:

$$V_1 = IR_1 = E \frac{R_1}{R_1 + R_2}$$

The Loop Method

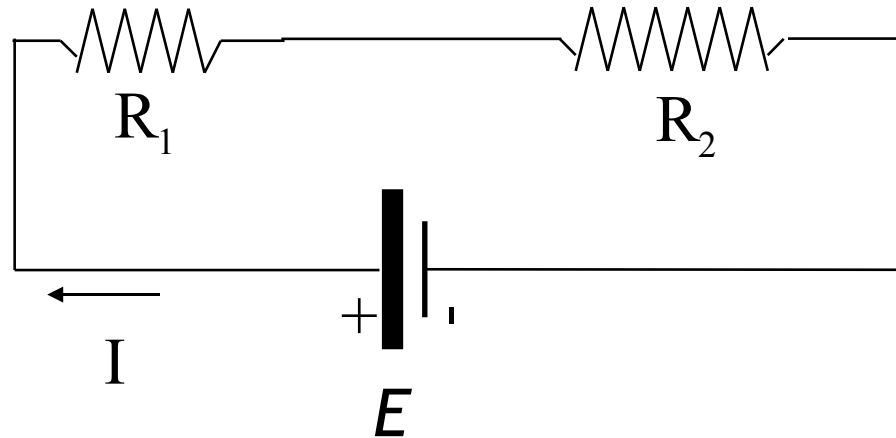

Go around the circuit in one direction.

If you pass a voltage source from $-$ to $+$,




\Rightarrow the voltage increases by E (or V).

As you pass a resistor the voltage decreases by $V = I R$.

The total change in voltage after a complete loop is zero.


Analyzing Resistor Networks

1. Replace resistors step by step.

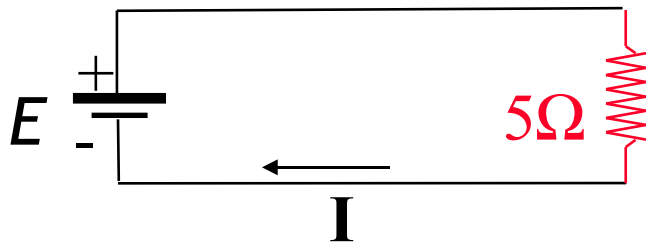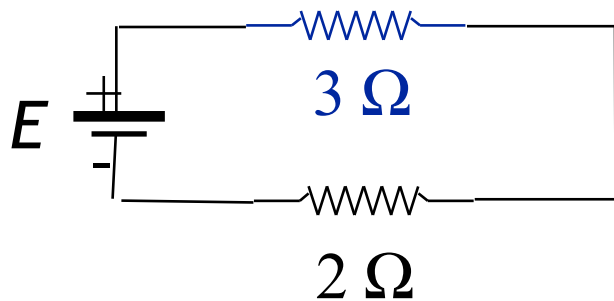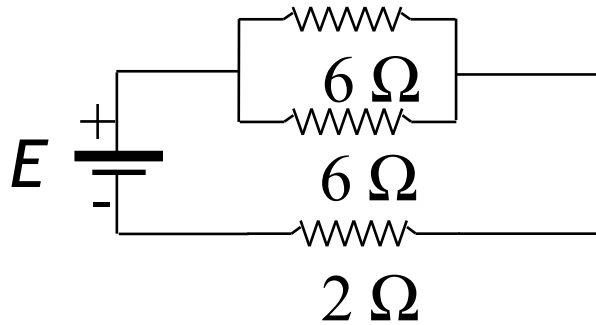

$$I = E / R$$

2. The loop method

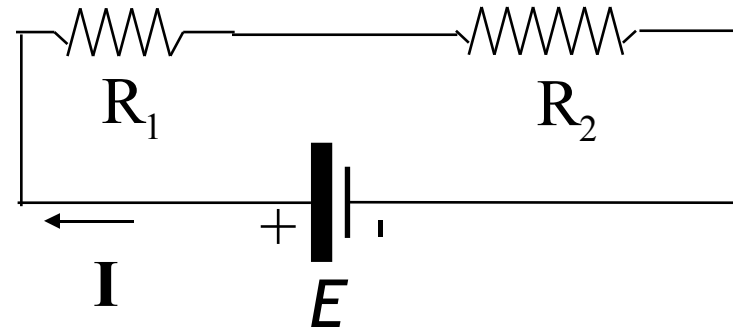


$$E - IR_1 - IR_2 = 0$$

$$E = I (R_1 + R_2)$$

$$I = E / (R_1 + R_2)$$


Analyzing Resistor Networks

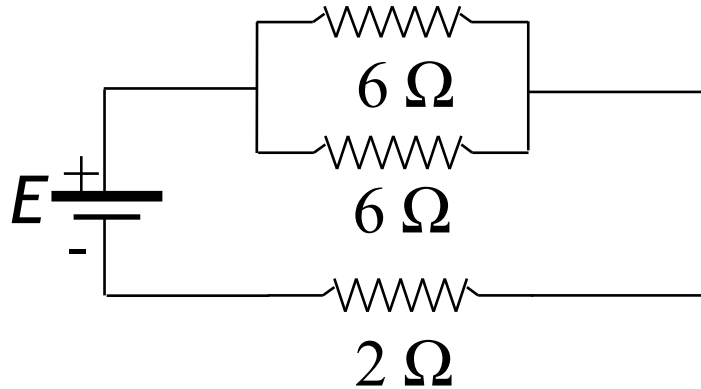Often you can replace sets of resistors step by step.




Analyzing Resistor Networks

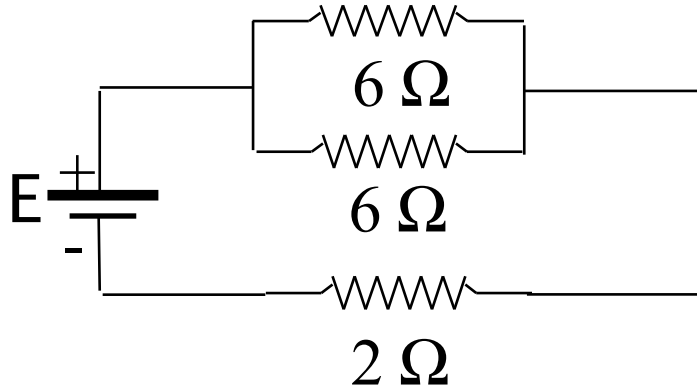Often you can replace sets of resistors step by step.




$$1/6 + 1/6 = 1/3$$

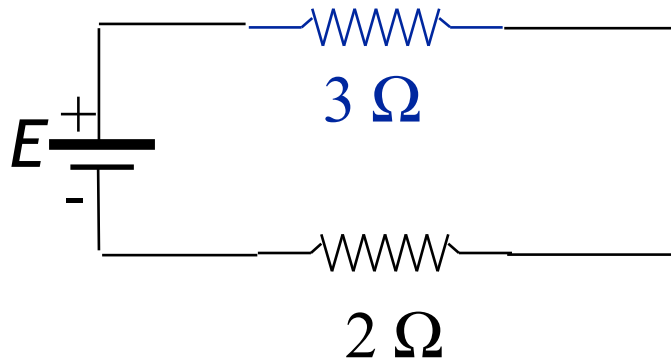

step 1



Analyzing Resistor Networks

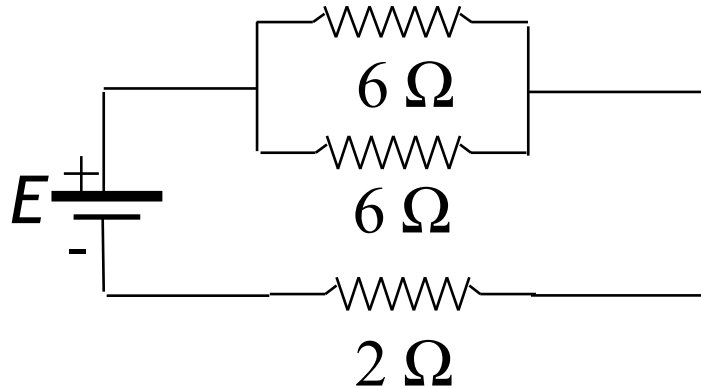Often you can replace sets of resistors step by step.



$$1/6 + 1/6 = 1/3$$


$$3 + 2 = 5$$

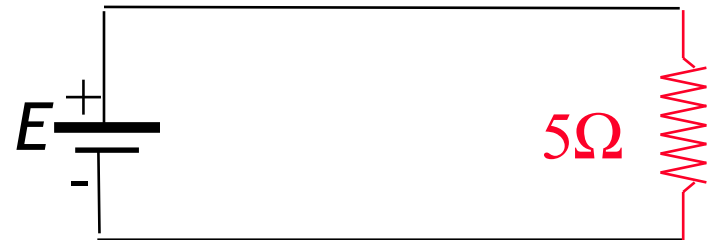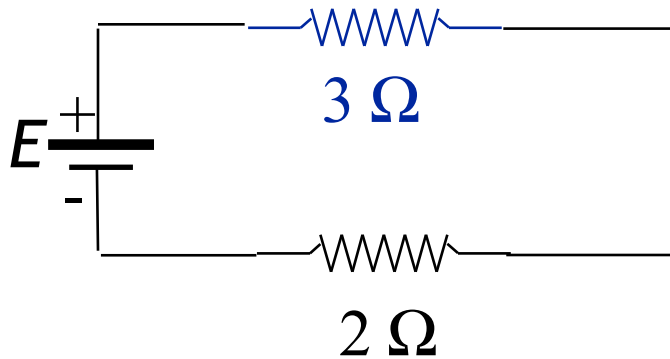

step 1


step 2

Internal Resistance of a Battery

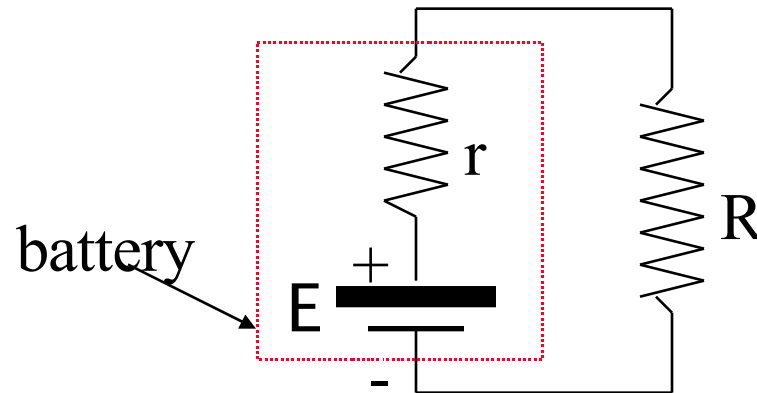

- One important point: batteries actually have an **internal resistance r**
- Often we neglect this, but sometimes it is significant.

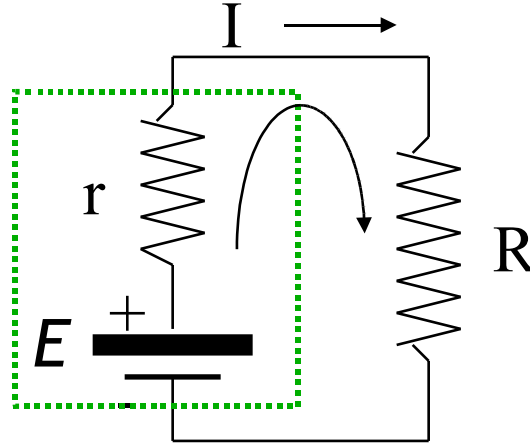Effect of Internal Resistance Analyzed by the Loop Method



Start at any point in the circuit. Go around the circuit in a loop. Add up (subtract) the potential differences across each element (keep the signs straight!).

$$E - Ir - IR = 0 \text{ (using } V=IR) \Rightarrow I = E / (R + r)$$


$$V_R = IR = ER / (R + r) = E / [1 + (r/R)]$$

$$\text{if } r \ll R \Rightarrow V_R = E$$


Kirchhoff's Laws

Kirchoff devised two laws that are universally applicable in circuit analysis:


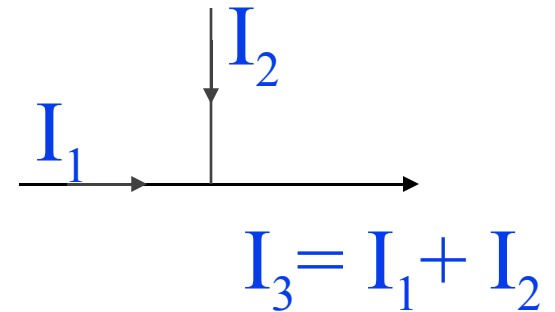
1. At any circuit junction, currents entering must equal currents leaving.



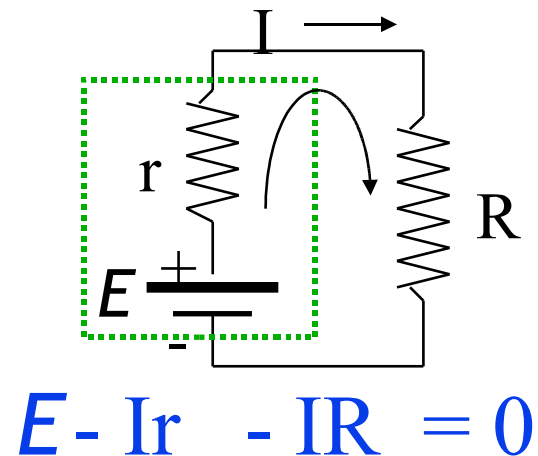2. Sum of all ΔV 's across all circuit elements in a loop must be zero.




RC Circuits: Charging

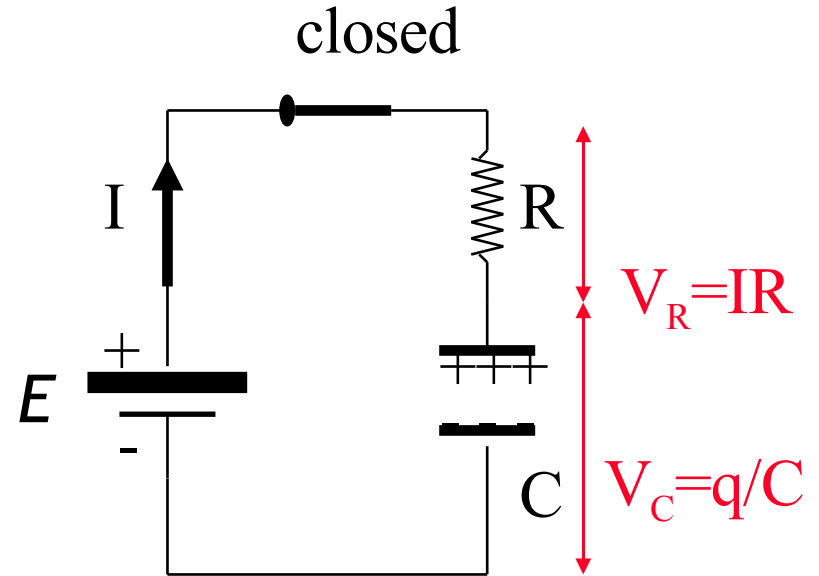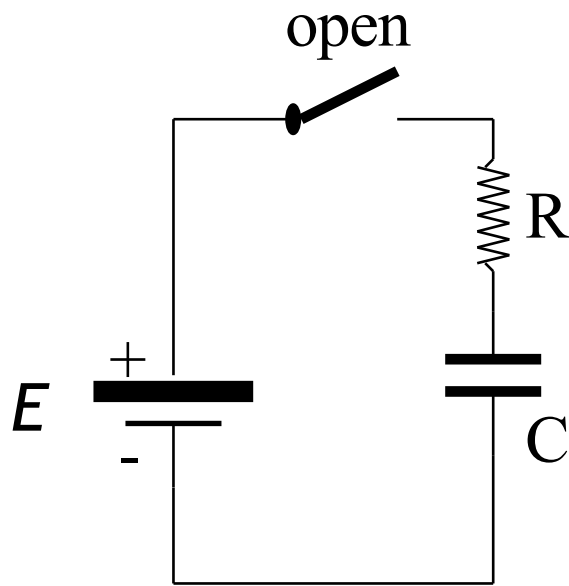

**When the switch closes, at first a high current flows:
 V_R is big and V_C is small.**

RC Circuits: Charging

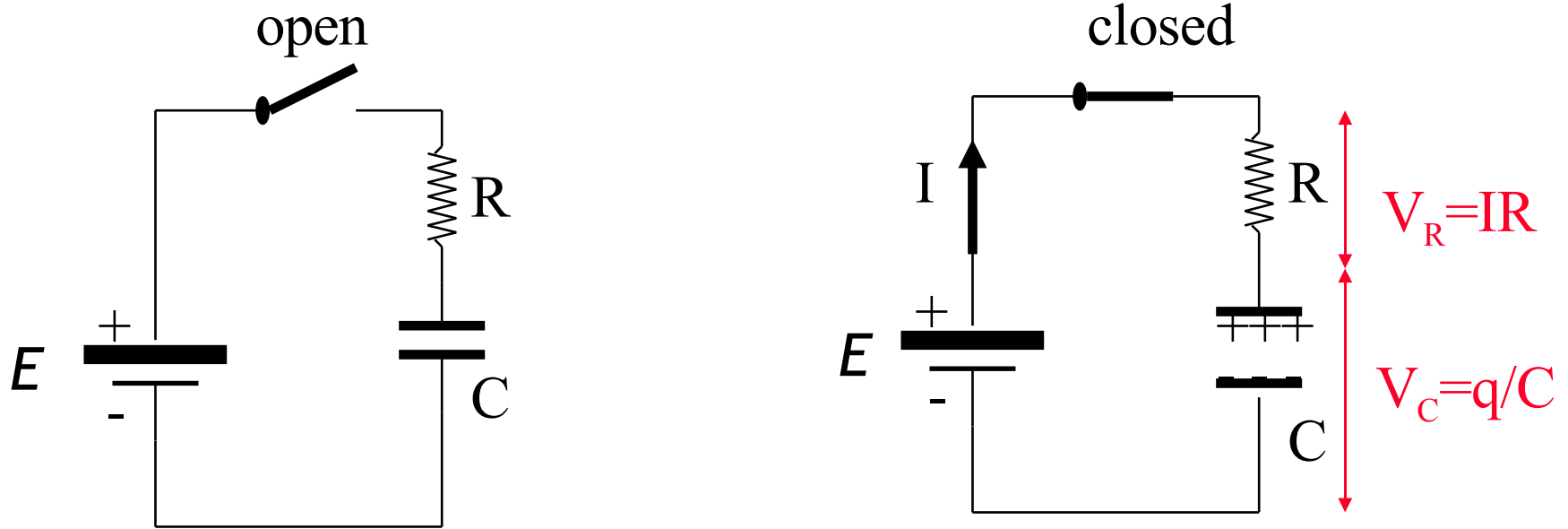


$$E = IR + Q/C$$

**When the switch closes, at first a high current flows:
 V_R is big and V_C is small.**

As q is stored in C , V_C increases.

This fights against the battery so I decreases.

RC Circuits: Charging

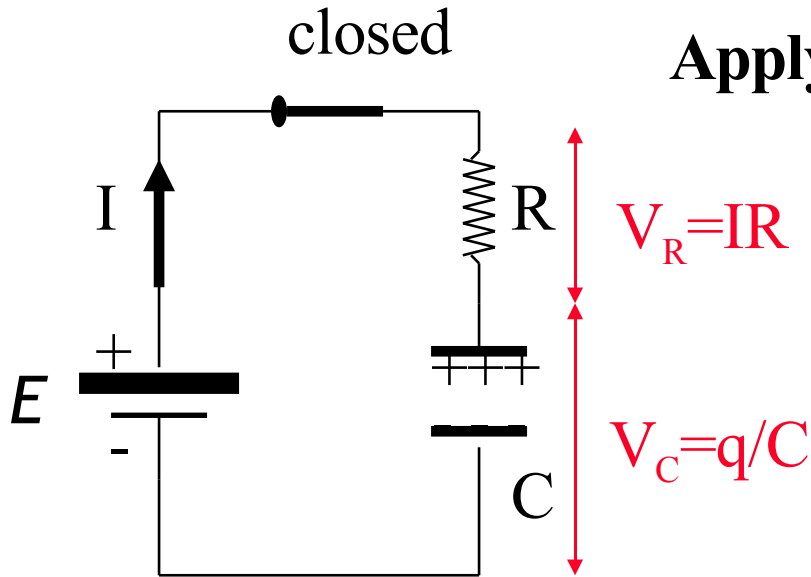

Apply the loop law: $E - IR - q/C = 0$

Take the derivative of this with respect to time:

$$-R \frac{dI}{dt} - \frac{1}{C} \frac{dq}{dt} = 0$$


Now use $dq/dt = I$ and rearrange:

$$\frac{dI}{dt} = -\frac{I}{RC}$$

This is a differential equation for $I(t)$.

It is solved subject to the initial condition $I(0) = E/R$.

RC Circuits: Charging

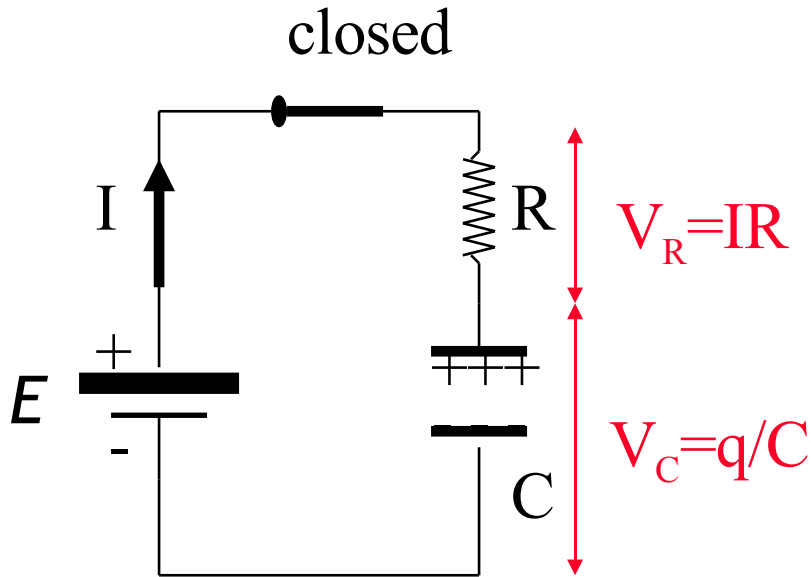

$$\frac{dI}{dt} = -\frac{I}{RC} \Rightarrow \frac{dI}{I} = -\frac{dt}{RC}$$


$$\int dI / I = - \int dt / (RC)$$

$$\ln I - \ln I(0) = -t / (RC)$$

$$I = I(0) \exp(-t / RC)$$

And $I(0) = E / R \Rightarrow I = \frac{E}{R} \exp(-t / RC)$

RC Circuits: Charging


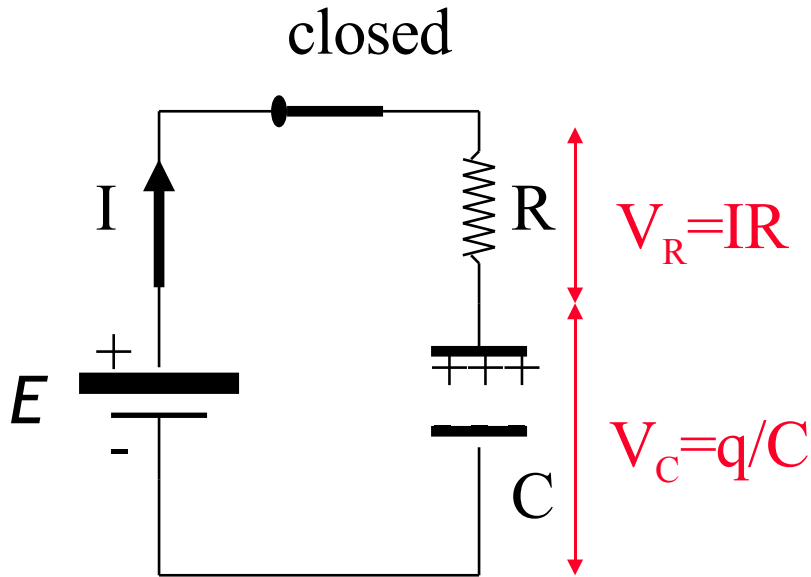


$$I = \frac{E}{R} \exp(-t / RC)$$


From this we get:

$$\left[\begin{array}{l} V_R = IR = E \exp(-t / RC) \\ V_C = E - V_R = E(1 - \exp(-t / RC)) \\ q = V_C C = EC(1 - e^{-t/RC}) \end{array} \right.$$


Charging

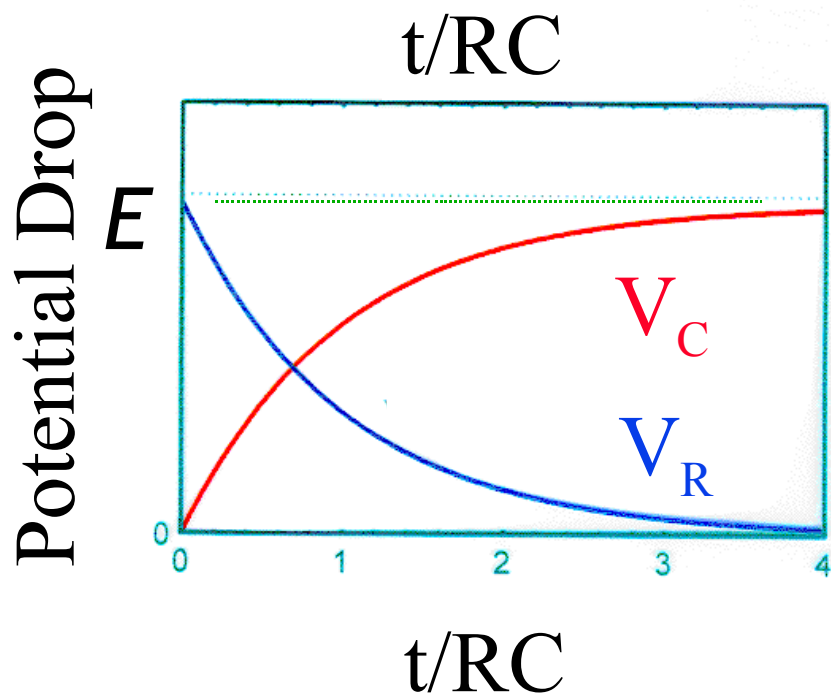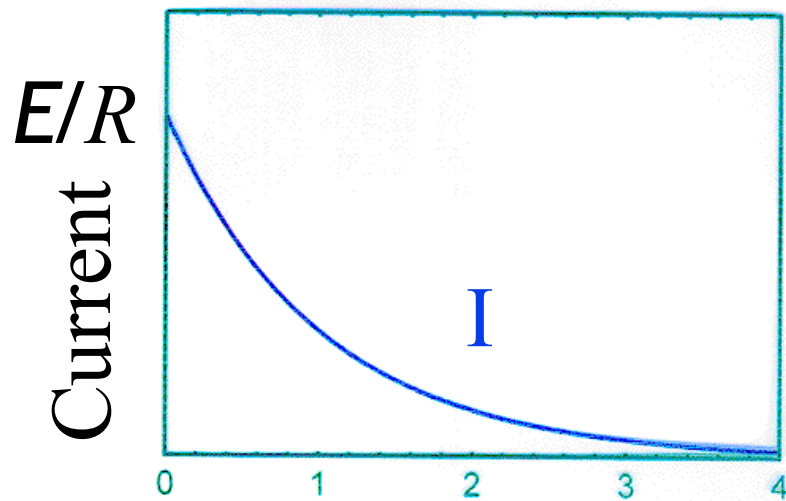

Discharging an RC Circuit

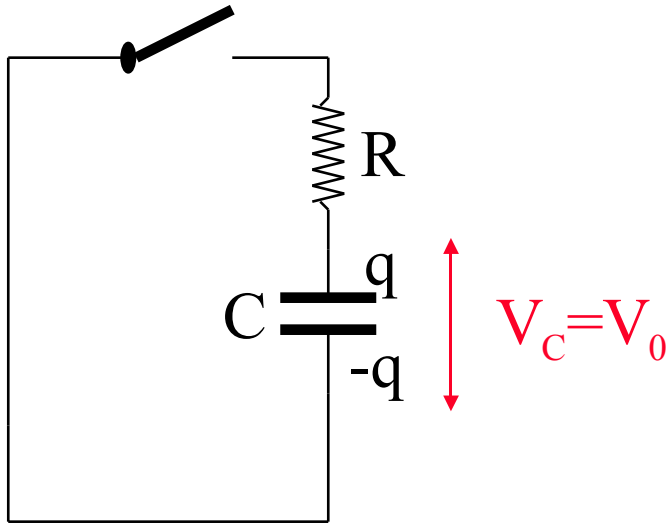


Open circuit

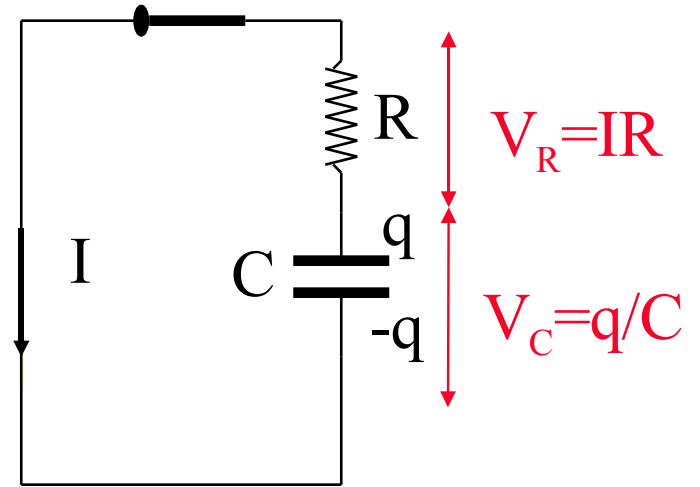


After closing switch

Discharging an RC Circuit

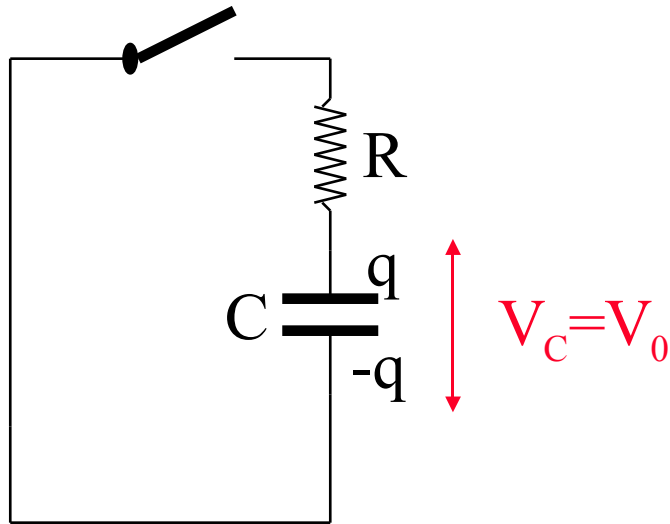

Open circuit

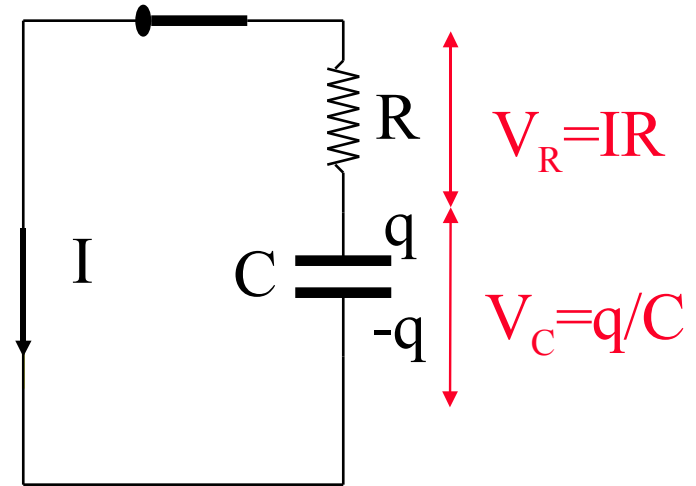


After closing switch


Current will flow through the resistor for a while.

Power $P = IV = I^2R$ will be dissipated in the resistor (as heat) while the current flows.

Discharging an RC Circuit

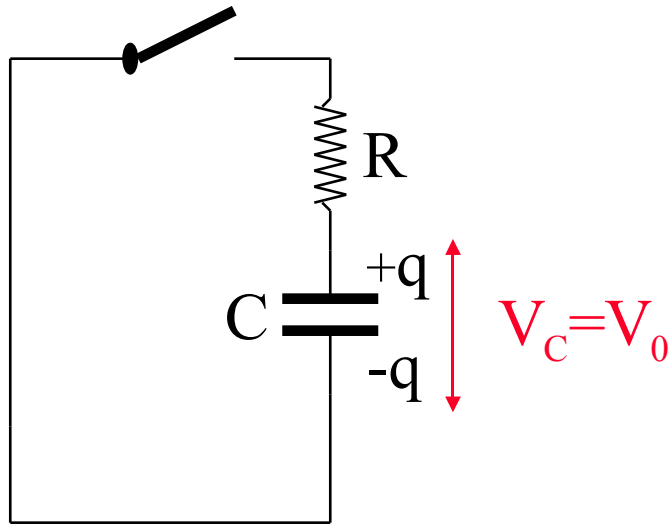

Open circuit

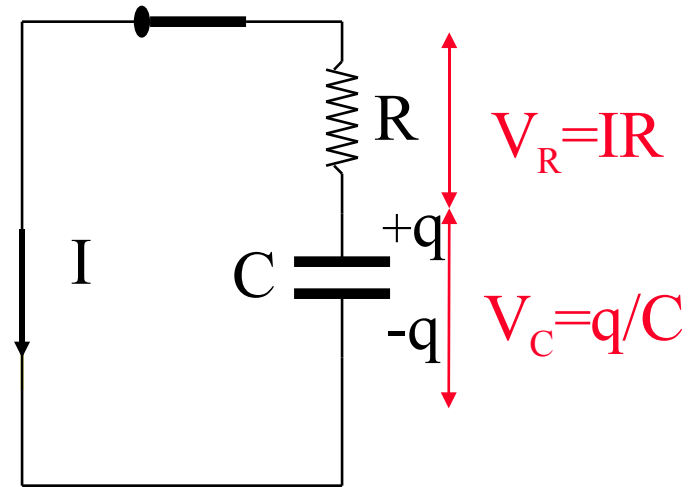


After closing switch

Current will flow through the resistor for a while. Eventually, the capacitor will lose all its charge, and the current will go to zero. During this transient:

$$q / C - I R = 0$$

Discharging an RC Circuit

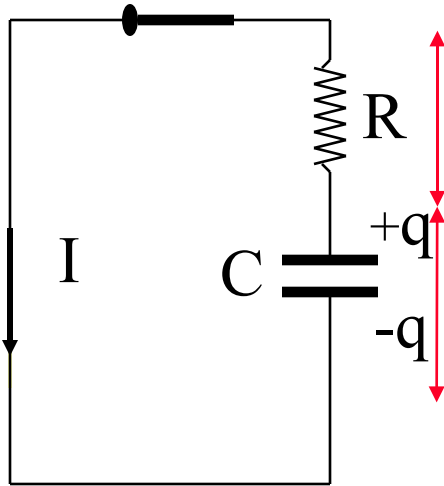

$$V_R = IR$$

$$V_C = q/C$$

Loop equation:

$$q/C - IR = 0 \Rightarrow I = q / (RC)$$

Take d/dt \Rightarrow
$$\frac{dI}{dt} = - \frac{I}{RC}$$

[Note that $I = - dq/dt$]


Here the current at $t=0$ is given by the initial voltage on the capacitor:

$$I(0) = V_0/R = q_0/RC$$

This equation is solved very much like the other (charging case):

$$I = \frac{V_0}{R} \exp(-t / RC)$$

Discharging an RC Circuit

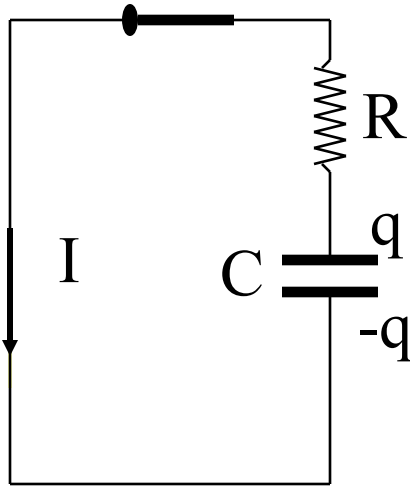

$$I = \frac{V_0}{R} \exp(-t / RC)$$



The charge on the capacitor is given by:

$$q/C - IR = 0 \quad \text{so} \quad q = C IR \quad [q = C V]$$

$$q = CV_0 \exp(-t / RC)$$

$$= q_0 \exp(-t / RC)$$


Discharging

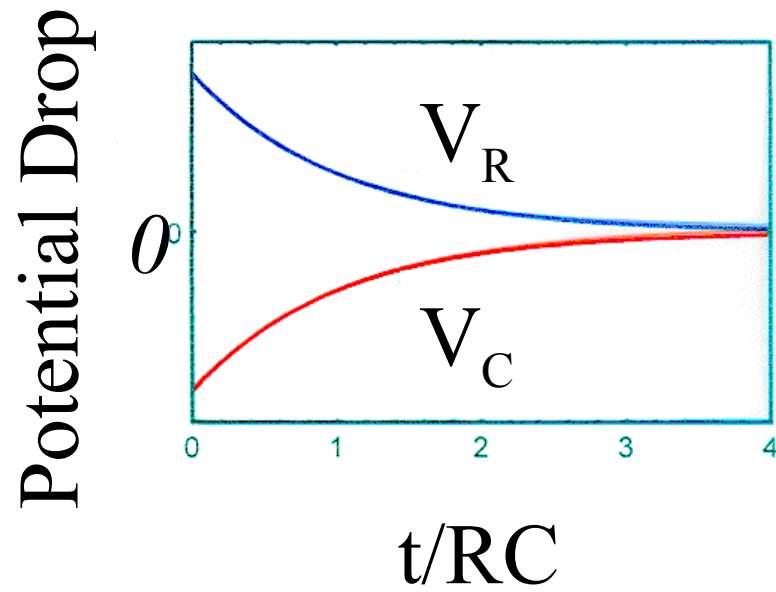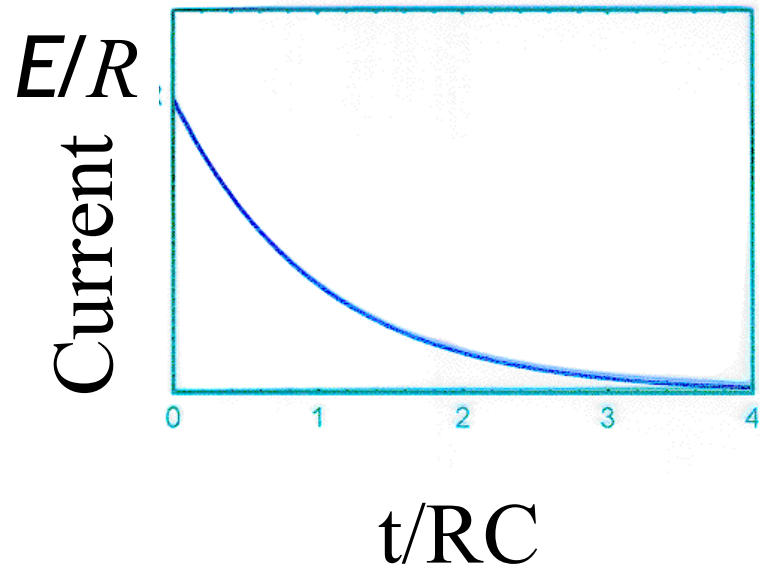

**Example: A capacitor C discharges through a resistor R.
(a) When does its charge fall to half its initial value ?**

Charge on a capacitor varies as

$$Q = Q_0 \exp(-t / RC)$$

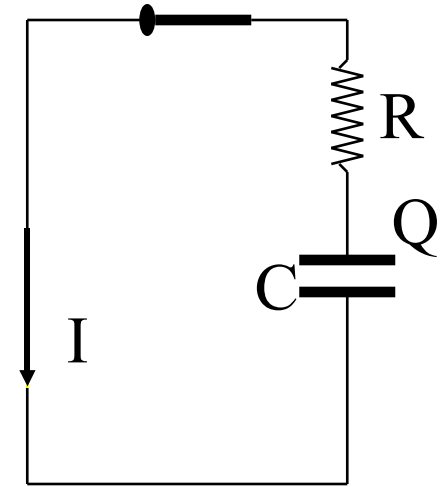


**Example: A capacitor C discharges through a resistor R.
(a) When does its charge fall to half its initial value ?**

Charge on a capacitor varies as

$$Q = Q_0 \exp(-t / RC)$$

Find the time for which $Q=Q_0/2$

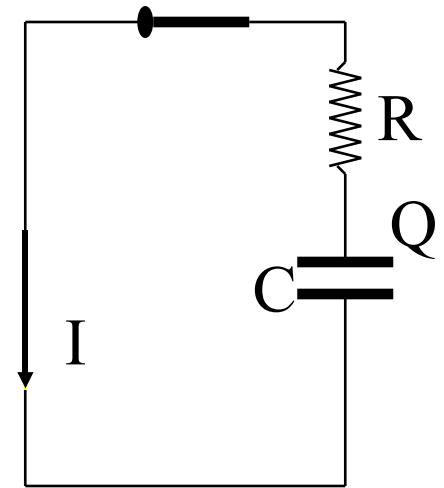


**Example: A capacitor C discharges through a resistor R.
(a) When does its charge fall to half its initial value ?**

Charge on a capacitor varies as

$$Q = Q_0 \exp(-t / RC)$$

Find the time for which $Q=Q_0/2$

$$\frac{1}{2} Q_0 = Q_0 \exp(-t / RC)$$

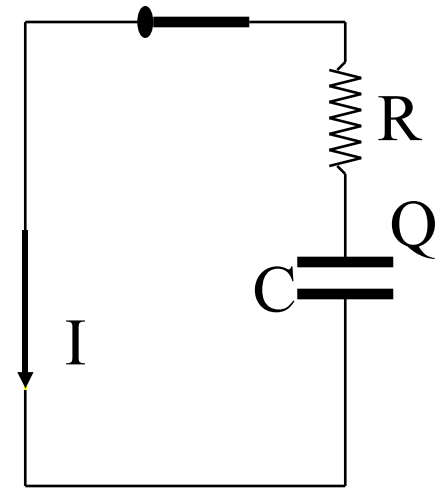

**Example: A capacitor C discharges through a resistor R.
(a) When does its charge fall to half its initial value ?**

Charge on a capacitor varies as


$$Q = Q_0 \exp(-t / RC)$$

Find the time for which $Q=Q_0/2$

$$\frac{1}{2} Q_0 = Q_0 \exp(-t / RC)$$

$$\therefore -\ln 2 = -\frac{t}{RC}$$

$$t = (\ln 2)RC = 0.69 RC$$

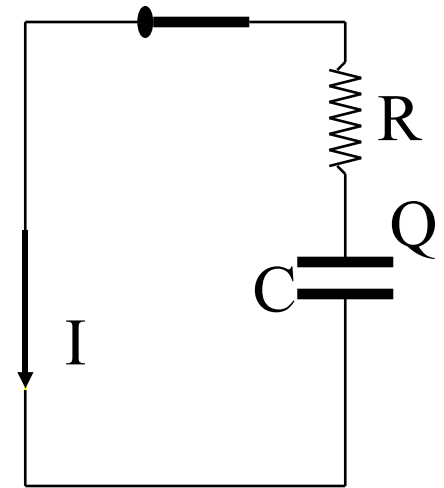

RC is the
“time constant”

**Example: A capacitor C discharges through a resistor R.
(b) When does the energy drop to half its initial value?**

The energy stored in a capacitor is

$$U(t) = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \exp(-2t / RC) = U_0 \exp(-2t / RC)$$

**Example: A capacitor C discharges through a resistor R.
(b) When does the energy drop to half its initial value?**

The energy stored in a capacitor is

$$U(t) = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \exp(-2t / RC) = U_0 \exp(-2t / RC)$$

We seek the time for U to drop to $U_0/2$:

$$\frac{1}{2} U_0 = U_0 \exp(-2t / RC)$$

**Example: A capacitor C discharges through a resistor R.
(b) When does the energy drop to half its initial value?**

The energy stored in a capacitor is

$$U(t) = \frac{Q^2}{2C} = \frac{Q_0^2}{2C} \exp(-2t / RC) = U_0 \exp(-2t / RC)$$

We seek the time for U to drop to $U_0/2$:

$$\frac{1}{2} U_0 = U_0 \exp(-2t / RC)$$

$$\therefore t = -\ln 2 = RC \frac{\ln 2}{2} = 0.35RC$$