

Inductance and Magnetic Energy

Chapter 32

Mutual Inductance


Self-Inductance

Inductors in Circuits


Magnetic Energy

Mutual Inductance

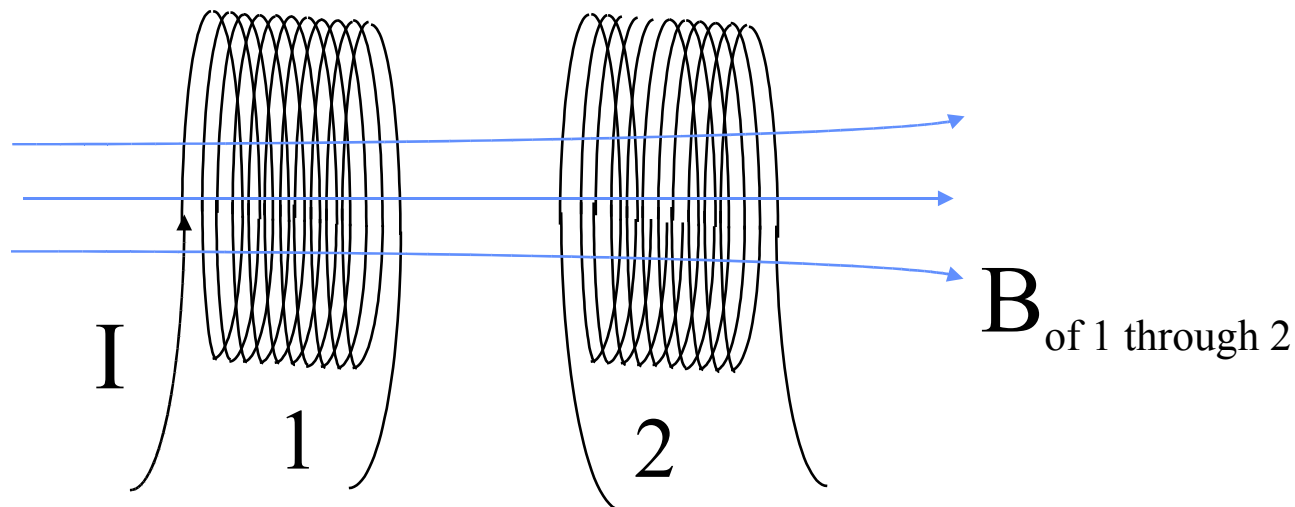- Two coils, 1 & 2, are arranged such that flux from one passes through the other.
- We already know that changing the current in 1 changes the flux (in the other) and so induces an emf in 2.
- This is mutual inductance.



Definition of the Mutual Inductance

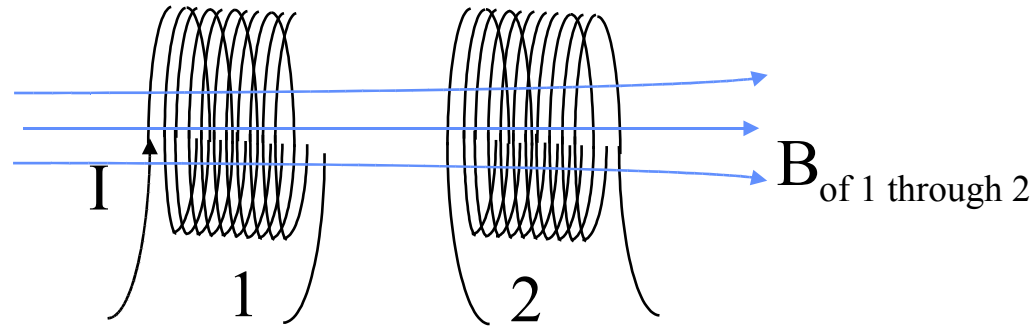

The *mutual inductance*, M , tells us how much flux through the second coil, Φ_2 , is caused by a current, I_1 , through the first:

$$M = \Phi_2 / I_1 \text{ which gives } \Phi_2 = M I_1$$

$$\text{so: } d\Phi_2 / dt = M dI_1 / dt$$

But by Faraday's law :

$$E_2 = - d\Phi_2 / dt = - M dI_1 / dt$$


Mutual Inductance is Geometric

- M arises from the way flux from one coil passes through the other: that is from the geometry and arrangement of the coils.
- Mutual means mutual. Note there is no subscript on M: the effect of 2 on 1 is identical to the effect of 1 on 2.
- Inductance has units: called the “Henry” (H).

$$1 \text{ H} = 1 \text{ Vs/A}$$

Self Inductance

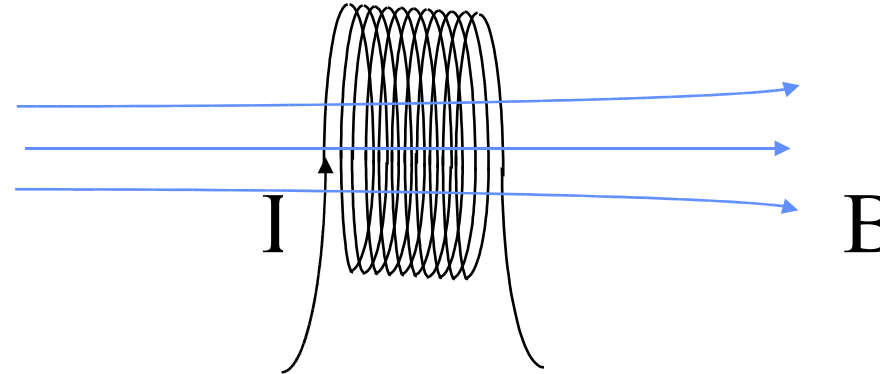A changing current in a coil can induce an emf in itself....



- If the current is steady: no problem, the coil acts like an ordinary piece of wire.
- But if the current changes, B changes and so then does Φ_B , and Faraday tells us there will be an induced emf.
- Lenz's law tells us that the induced emf must be in such a direction as to produce a current which makes a magnetic field opposing the change.

Implications of Self Inductance

- Define the self inductance of a circuit element (a coil, wire, resistor or whatever) as

$$L = \Phi_B / I$$

- From this we have $\Phi_B = LI$ and so

$$d \Phi_B / dt = L dI / dt$$

- and Faraday's law gives

$$E = - L dI / dt$$

- Since this emf opposes changes in the current (in the component) it is often called the “back emf”.
- From now on “inductance” means self-inductance.

Example: Finding Inductance

What is the (self) inductance of a solenoid ($L = \Phi_B/I$) with area A , length d , and n turns per unit length?

In the solenoid $B = \mu_0 n I$, so the flux through one turn is: $\phi_B = BA = \mu_0 n I A$

The total flux in the solenoid is $(nd)\phi_B$

Therefore, $\Phi_B = \mu_0 n^2 I A d$ and so $L = \Phi_B/I$ gives

$$L = \mu_0 n^2 A d$$


(only geometry)

Inductance Affects Circuits and Stores Energy

- This has important implications.....
- First an observation: Since E cannot be infinite neither can dI/dt . Therefore, current *cannot change instantaneously*.
- We will see that inductance in a circuit affects current in somewhat the same way that capacitance in a circuit affects voltage.
- A ‘thing’ (a component) with inductance in a circuit is called an **inductor**.

Circuits With Inductance

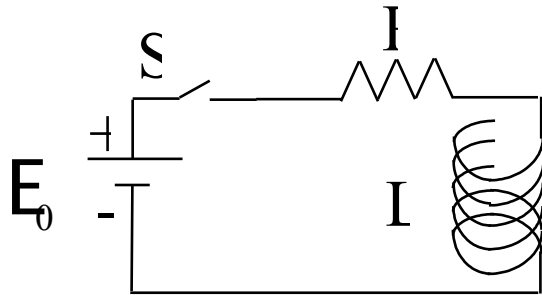
We start with a simple circuit containing a battery, a switch, a resistor, and an inductor, and follow what happens when the switch is closed.




While the switch is open current can't flow.

Circuits With Inductance

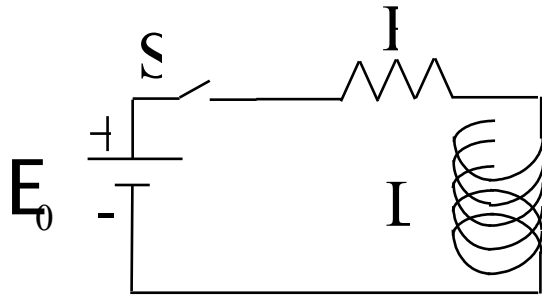We start with a simple circuit containing a battery, a switch, a resistor, and an inductor, and follow what happens when the switch is closed.



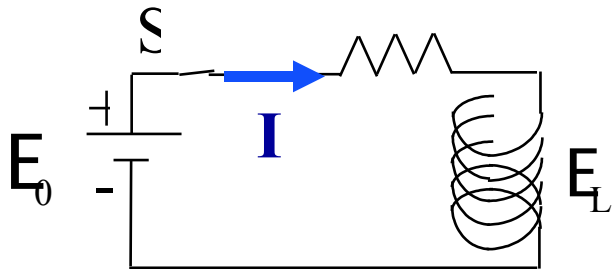While the switch is open current can't flow.




When the switch is closed current I flows, growing gradually, and a 'back emf' E_L is generated in inductor.

The emf E_L opposes the current I


$$\Rightarrow E_L = -L \frac{dI}{dt}$$

Circuits With Inductance

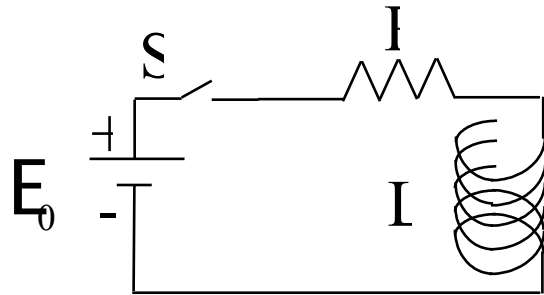
We start with a simple circuit containing a battery, a switch, a resistor, and an inductor, and follow what happens when the switch is closed.



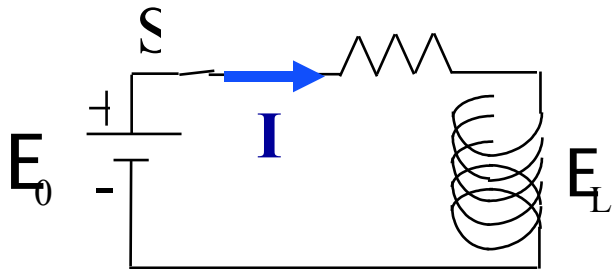While the switch is open current can't flow.



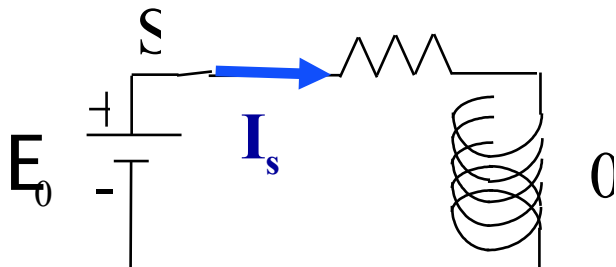
When the switch is closed current I flows, growing gradually, and a 'back emf' \mathcal{E}_L is generated in inductor.




The emf \mathcal{E}_L opposes the current I
 $\Rightarrow \mathcal{E}_L = -L \frac{dI}{dt}$
After a long time the current becomes steady. Then \mathcal{E}_L is zero.

Circuits With Inductance


When the switch S is closed

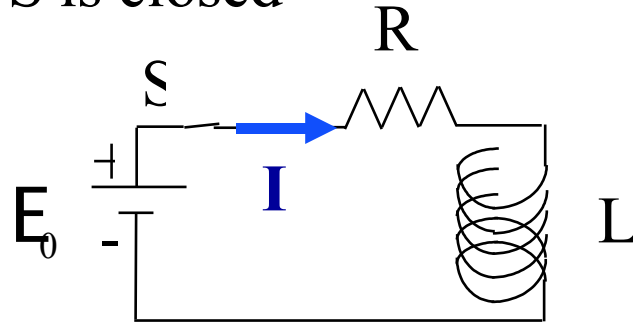

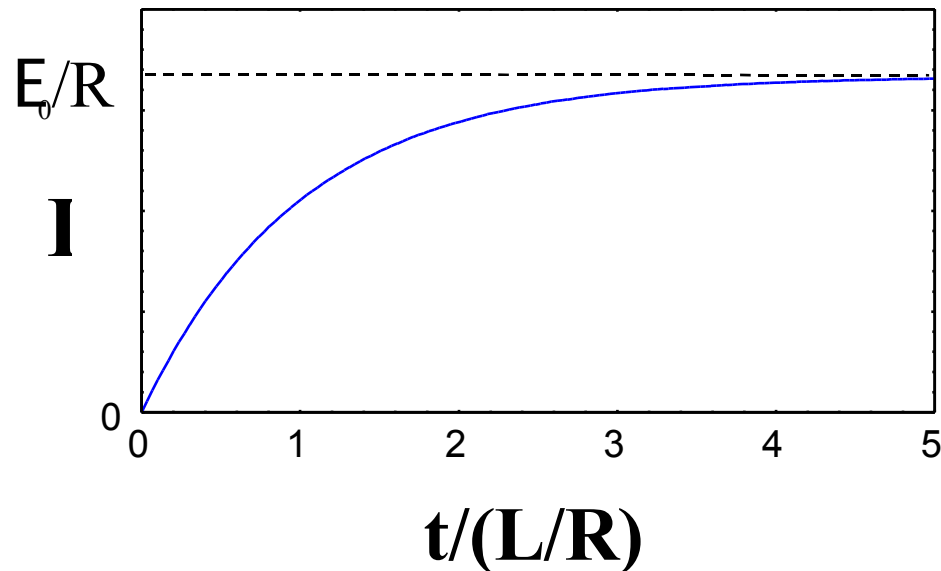The current I increases exponentially from $I = 0$ to $I = E_0/R$



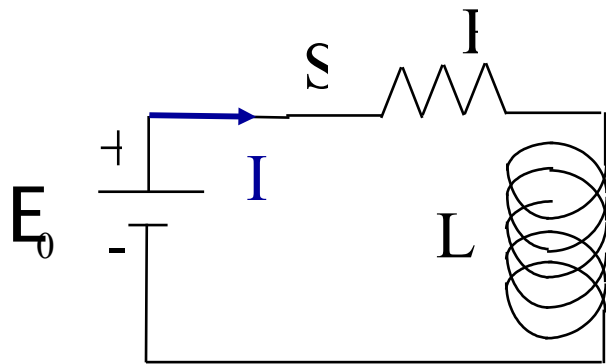Analysis of the Establishment of a Current



We use the loop method

$$E_0 - IR + E_L = 0 \Rightarrow E_0 - IR - L \frac{dI}{dt} = 0$$

$$IR = E_0 - L \frac{dI}{dt} \Rightarrow R(I - (E_0/R)) = -L \frac{dI}{dt}$$


$$dI / (I - (E_0/R)) = - dt / (L/R) \Rightarrow \int dI / (I - (E_0/R)) = - \int dt / (L/R)$$

$$\ln (I - (E_0/R)) - \ln -(E_0/R) = - t / (L/R) \Rightarrow \ln (-I/(E_0/R) + 1) = - t / (L/R)$$


$$-I/(E_0/R) + 1 = \exp (- t / (L/R)) \Rightarrow I/(E_0/R) = 1 - \exp (- t / (L/R))$$

$$I = (E_0/R) [1 - \exp (- t / (L/R))]$$

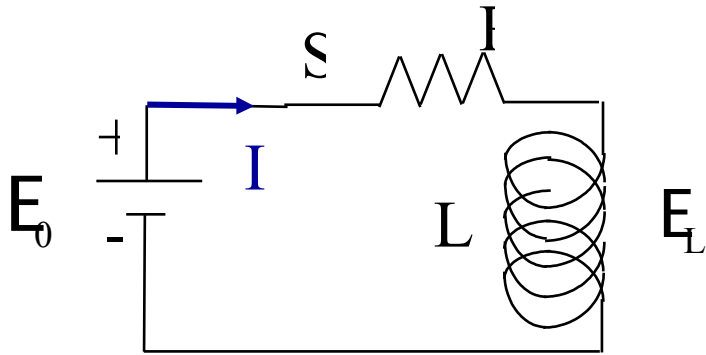Analysis of the Establishment of a Current



$$I = (E_0/R) [1 - \exp(-t / (L/R))]$$

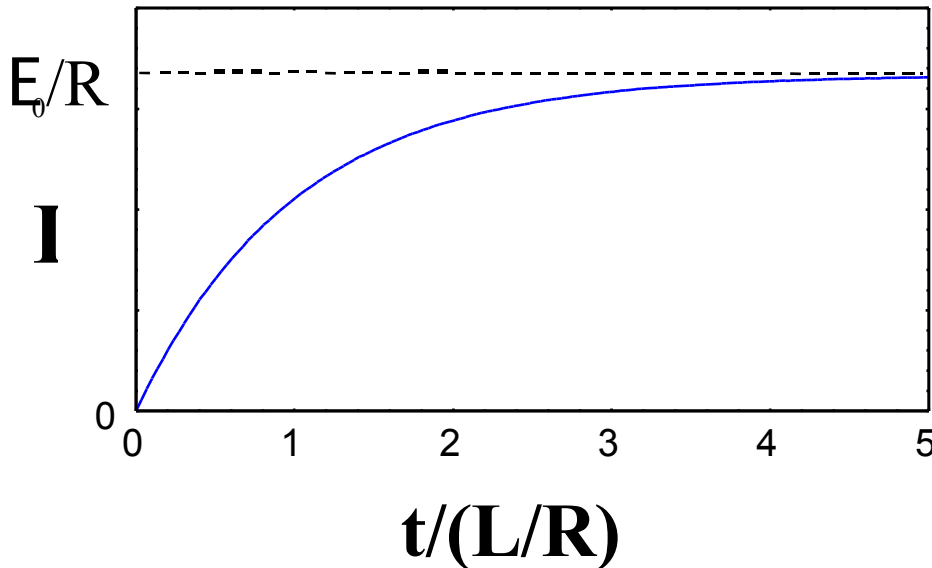


The current increases
exponentially
with time constant

$$\tau = L / R$$

$$t = 0 \Rightarrow I = 0$$

$$t = \infty \Rightarrow I = E_0/R$$


Inductor's emf \mathcal{E}_L

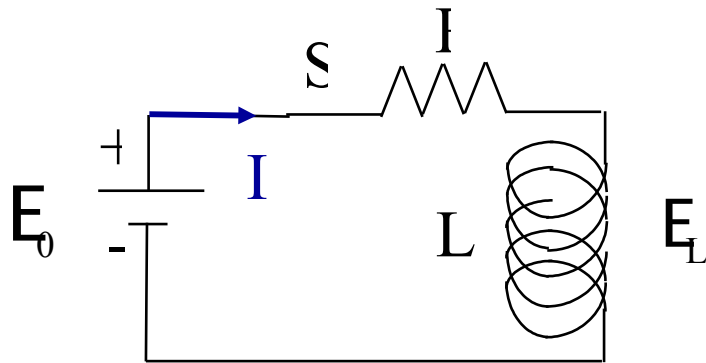

$$\mathcal{E}_L = -L \left(\frac{dI}{dt} \right)$$

$$I = \left(\frac{\mathcal{E}_0}{R} \right) \left[1 - \exp \left(-t / \left(\frac{L}{R} \right) \right) \right]$$
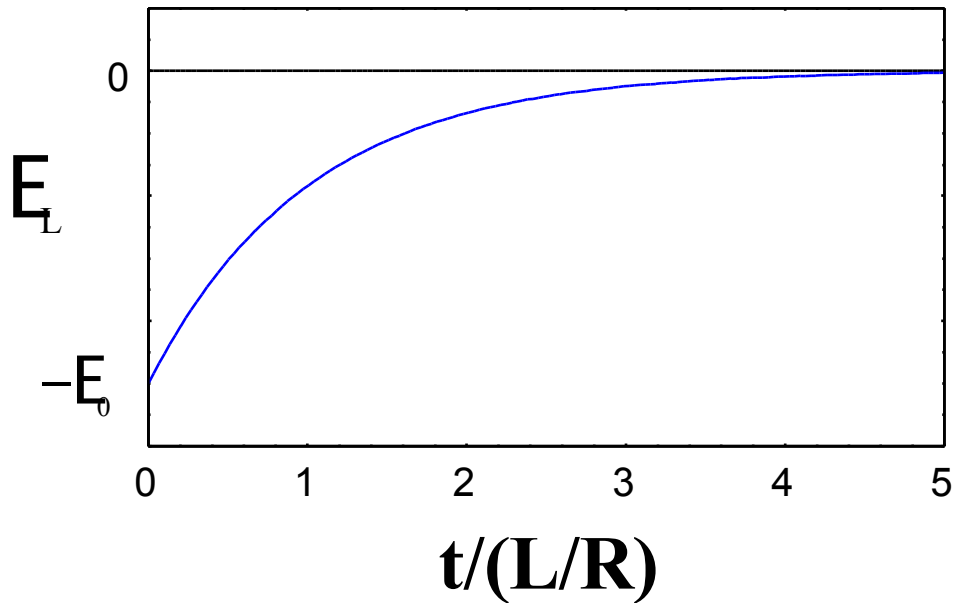
$$\mathcal{E}_L = L \left(\frac{\mathcal{E}_0}{R} \right) \left(-\frac{R}{L} \right) \exp \left(-t / \left(\frac{L}{R} \right) \right)$$




$$\mathcal{E}_L = -\mathcal{E}_0 \exp \left(-t / \left(\frac{L}{R} \right) \right)$$



$$t = 0 \Rightarrow \mathcal{E}_L = -\mathcal{E}_0$$

$$t = \infty \Rightarrow \mathcal{E}_L = 0$$

Plots for the “RL” Circuit

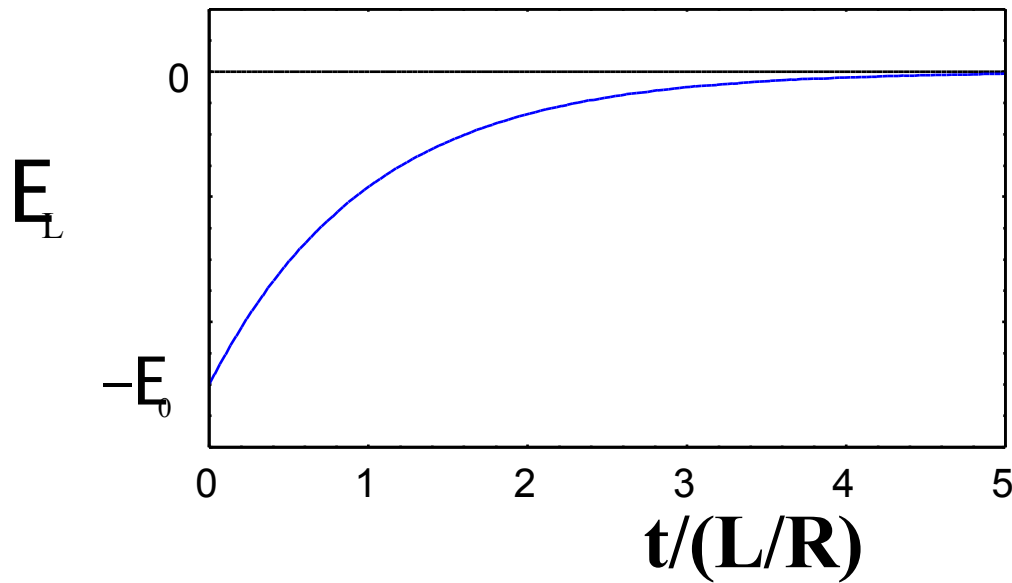


$$E_L = - E_0 \exp (- t / (L/R))$$

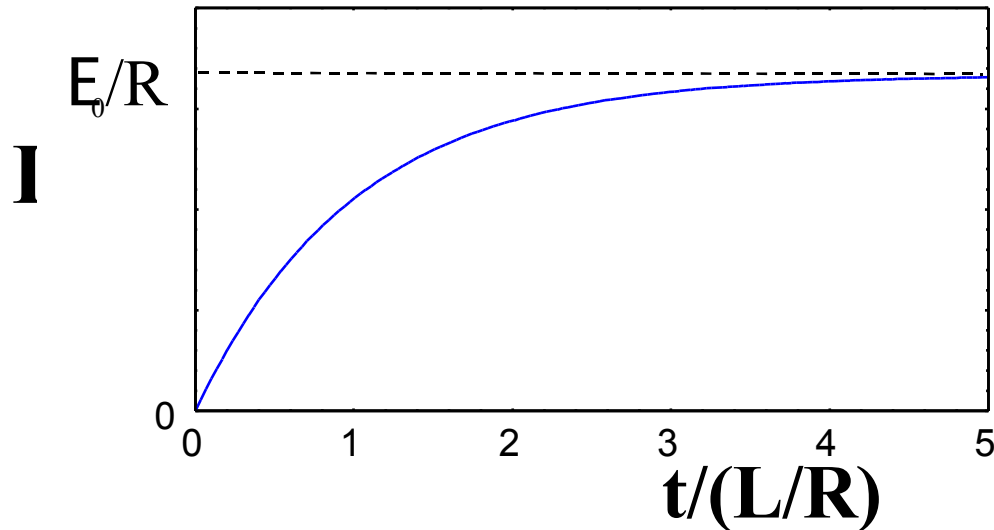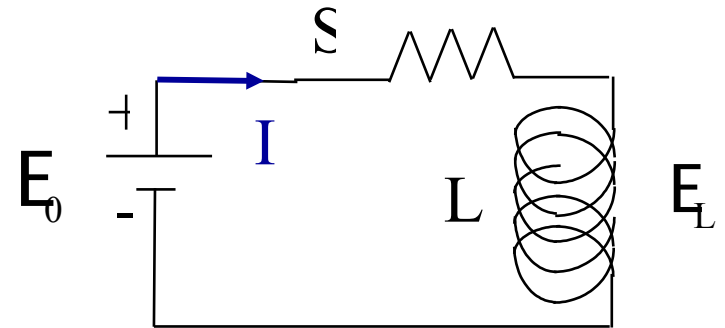

$$I = (E_0/R) [1 - \exp (- t / (L/R))]$$

Decay of an “RL” Circuit

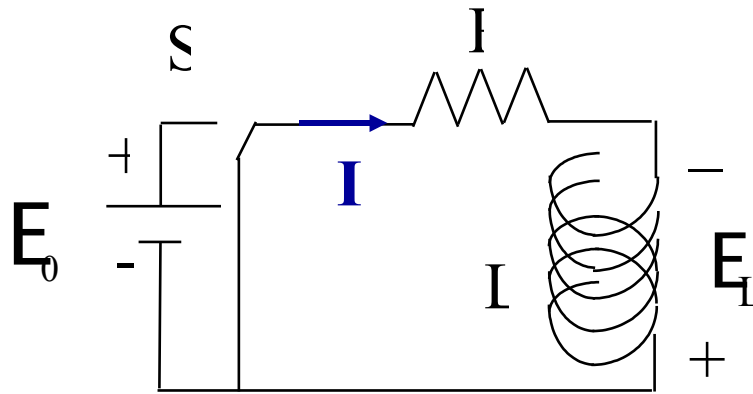


- After I reaches E_0/R move the switch as shown.
- The loop method gives $E_L - IR = 0$ or $E_L = IR$
- Remember that $E_L = -L \, dI/dt \Rightarrow -L \, dI/dt = IR$
 $dI/I = - dt / (L/R) \Rightarrow \int dI/I = - \int dt / (L/R)$
- $\ln I_0/I = - t / (L/R) \Rightarrow I = I_0 \exp [- t / (L/R)]$
- But $I_0 = E_0/R$
- Then: $I = (E_0/R) \exp [- t / (L/R)]$

Inductors in Circuits

- The presence of inductance prevents currents from changing instantaneously.
- The time constant of an “RL” circuit is $\tau = L/R$.
- Next we will see that inductors store energy because they confine magnetic fields.
(This is very similar to the idea that capacitors store energy in the confined electric fields.)

Energy Stored in an Inductor

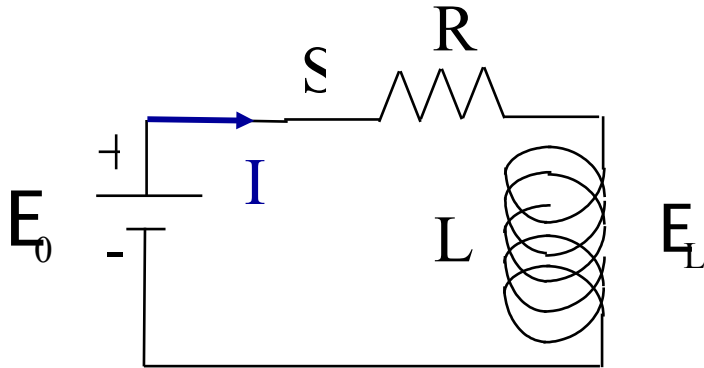

Recall the original circuit when current was changing (building up). The loop method gave: $E_0 - IR + E_L = 0$

Multiply by I , and use Faraday's law for E_L ($E_L = -L dI/dt$)

Then:

$$IE_0 - I^2R - ILdI/dt = 0$$

or:

$$IE_0 - I^2R - d[(1/2)LI^2]/dt = 0 \quad \{d[(1/2)LI^2]/dt = ILdI/dt\}$$

- Think about $I\mathcal{E}_0 - I^2R - d((1/2)LI^2)/dt = 0$
- $I\mathcal{E}_0$ is the power (energy per unit time) delivered by the battery.
- I^2R is the power dissipated in the resistor.

- Think about $IE_0 - I^2R - d((1/2)LI^2)/dt = 0$
- IE_0 is the power (energy per unit time) delivered by the battery.
- I^2R is the power dissipated in the resistor.
- Hence we'd like to interpret $d((1/2)LI^2)/dt$ as the rate at which energy is stored in the inductor.
 - In creating the magnetic field in the inductor we are storing energy

- Think about $IE_0 - I^2R - d((1/2)LI^2)/dt = 0$
- IE_0 is the power (energy per unit time) delivered by the battery.
- I^2R is the power dissipated in the resistor.
- Hence, we'd like to interpret $d[(1/2)LI^2]/dt$ as the rate at which energy is stored in the inductor.
 - In creating the magnetic field in the inductor we are storing energy
- The amount of energy in the magnetic field is:

$$U_B = \frac{1}{2} LI^2$$

Energy Density in a Magnetic Field

- We have shown $U_B = \frac{1}{2} LI^2$ (solenoid).
- Therefore,

$$U_B = \frac{1}{2} \mu_o n^2 A \ell I^2 = \frac{A \ell}{2 \mu_o} (\mu_o^2 n^2 I^2) = \frac{A \ell}{2 \mu_o} B^2$$

- Since $A \ell$ is the volume of the solenoid, the stored energy density is:

$$u_B = B^2 / (2 \mu_o)$$

- This turns out to be the

energy density in a magnetic field

Summary

- We defined mutual and self inductance,
- Calculated the inductance of a solenoid.
- Saw the effect of inductance in “RL” circuits.
- Developed an expression for the stored energy.
- Derived an expression for the energy density of a magnetic field.
- Next class we will start learning about alternating-current (AC) circuits, containing resistors, capacitors, and inductors.